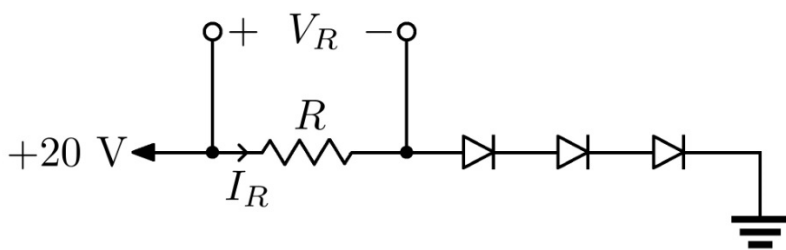


① (from 2022 midterm)


(● points) Consider the circuit shown below, consisting of a resistor (with resistance R) and three diodes. The voltage drop across the resistor is denoted as V_R , while the current through the resistor is denoted as I_R . Use the constant-voltage-drop model for the diodes (with $V_D = 0.7\text{ V}$) to answer the following questions.



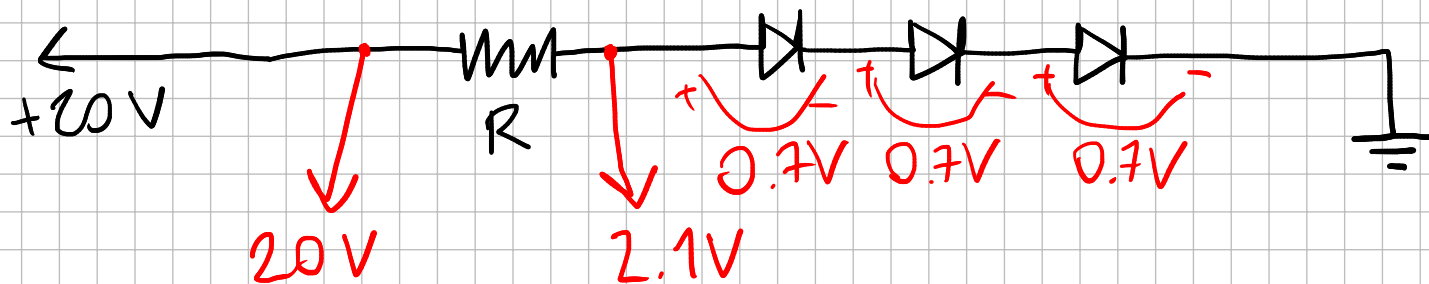a) Find the value of V_R .

solution:

Using the constant-voltage-drop model with $V_D = 0.7\text{ V}$, we observe:



$$\text{Thus: } V_R = 20\text{ V} - 2.1\text{ V} = 17.9\text{ V} \quad \checkmark$$


b) Using the value of V_R found in a), find the value of R for which I_R is equal to 2 A.

solution: Writing Ohm's law for the resistor:

$$R = \frac{V_R}{I_R} = \frac{17.9\text{ V}}{2\text{ A}} = 8.95\ \Omega \quad \checkmark$$

② (from 2022 midterm)

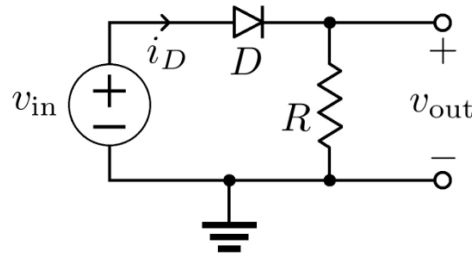
(10 points) Consider the circuit shown below, consisting of a resistor (with a resistance of $R = 100 \Omega$) and a diode D . The input voltage is denoted as v_{in} , while the diode current is denoted as i_D . The output voltage is the voltage drop across the resistor, and it is denoted as v_{out} .



A symmetrical square wave of 10 V peak amplitude and zero average is applied to the circuit as v_{in} . Use the constant-voltage-drop model for the diode (with $V_D = 0.7 \text{ V}$) to answer the following questions.

a) Find the resulting average value of v_{out} .

solution:

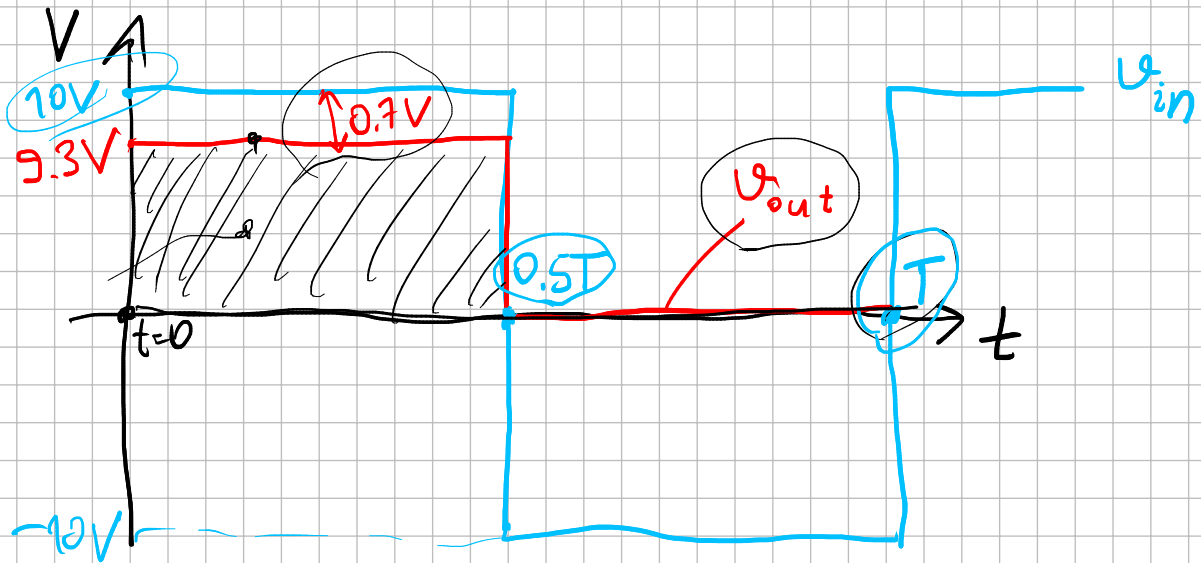

$$\text{average}(v_{out}) \triangleq \frac{\int_0^T v_{out} dt}{T}$$

$$= \frac{9.3\text{V} \cdot 0.5T}{T} = 4.65\text{V}$$

b) Find the resulting peak value of i_D .

solution: Writing Ohm's law for the resistor:


$$i_D(t) = \frac{v_{out}(t)}{R}$$

\Leftrightarrow

$$\text{peak}(i_D) = \frac{\text{peak}(v_{out})}{R} = \frac{9.3\text{V}}{100\Omega} = 93\text{mA}$$

③ (from 2022 midterm)

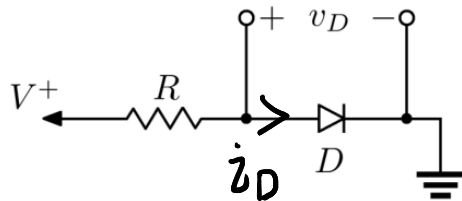~~10~~ points) Consider the circuit shown below, consisting of a resistor (with resistance $R = 20\text{ k}\Omega$) and a diode. The voltage drop across the diode is denoted as v_D .



The power supply V^+ has a dc value of 20.7 V, and a 60-Hz sinusoid of 2-V peak amplitude superimposed on this dc value. Assume the diode to have a 0.7-V drop at 1-mA current and answer the following questions.

a) Find the dc value of the diode current.

solution: Writing Ohm's law for the resistor:

$$i_D(t) = \frac{V^+(t) - v_D(t)}{R}$$

\Leftrightarrow

$$\text{dc}(i_D) = \frac{\text{dc}(V^+) - V_D}{R} = \frac{20.7\text{V} - 0.7\text{V}}{20\text{ k}\Omega} = 1\text{mA}$$

assume that this is 0.7V

assumption is correct


b) Find the peak amplitude of the sine-wave voltage signal appearing across the diode.

Solution:

diode incremental resistance:

$$\text{(for } I_D = 1\text{mA)} \quad r_d = \frac{V_T}{I_D} = \frac{25\text{mV}}{1\text{mA}} = 25\Omega$$

Small-signal equivalent circuit:

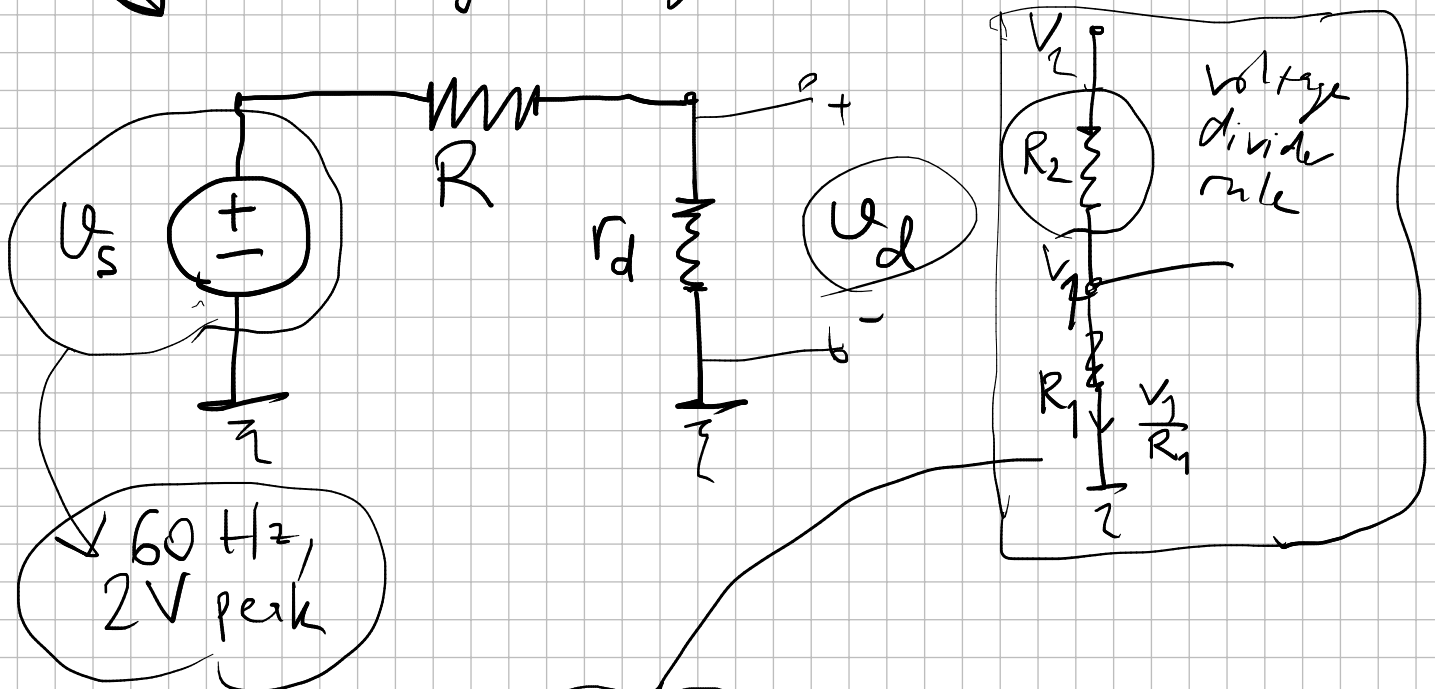

$$U_d = U_s \cdot \frac{r_d}{R + r_d}$$

$$\text{peak}(U_d) = \text{peak}(U_s) \cdot \frac{r_d}{R + r_d}$$

$$\text{peak}(U_d) = 2\text{V} \cdot \frac{25\Omega}{20\text{k}\Omega + 25\Omega} = 2.5\text{mV}$$

④ (from 2022 midterm)

(● points) Consider a MOSFET (n -channel enhancement-type) with the following parameters: $W/L = 12$, $t_{\text{ox}} = 6 \text{ nm}$, $\epsilon_{\text{ox}} = 3.45 \times 10^{-11} \text{ F/m}$, $\mu_n = 450 \text{ cm}^2/\text{Vs}$, and $V_t = 0.7 \text{ V}$.

- (a) (● points) Find the value of V_{GS} (voltage between the gate and the source) needed to operate the MOSFET in the saturation region with a dc current of $120 \mu\text{A}$.
- (b) (● points) Find the value of V_{OV} (overdrive voltage) required to make the MOSFET operate as a $2000\text{-}\Omega$ resistor for very small v_{DS} (voltage between the drain and the source).

Solution (a):

$$C_{\text{ox}} = \frac{\epsilon_{\text{ox}}}{t_{\text{ox}}} = \frac{3.45 \times 10^{-11} \text{ F/m}}{6 \times 10^{-9} \text{ m}} = 5.75 \times 10^{-3} \text{ F/m}^2$$

$$k'_n = \mu_n C_{\text{ox}} = (450 \text{ cm}^2/\text{Vs}) \times (5.75 \times 10^{-3} \text{ F/m}^2) = 258.75 \times 10^{-6} \text{ F}/(\text{V s})$$

For operation in the saturation region:

$$i_D = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2$$

$$120 \times 10^{-6} \text{ A} = \frac{1}{2} \times (258.75 \times 10^{-6} \text{ F}/(\text{V s})) \times 12 \times V_{OV}^2$$

$$V_{OV} = 0.28 \text{ V}$$

$$V_{GS} = V_t + V_{OV} = 0.7 \text{ V} + 0.28 \text{ V} = 0.98 \text{ V}$$

Solution (b):


For the MOSFET with v_{DS} very small

$$r_{DS} = \frac{1}{k'_n \frac{W}{L} V_{OV}}$$

$$2000 \text{ }\Omega = \frac{1}{(258.75 \times 10^{-6} \text{ F}/(\text{V s})) \times 12 \times V_{OV}}$$

$$V_{OV} = 0.16 \text{ V}$$

5

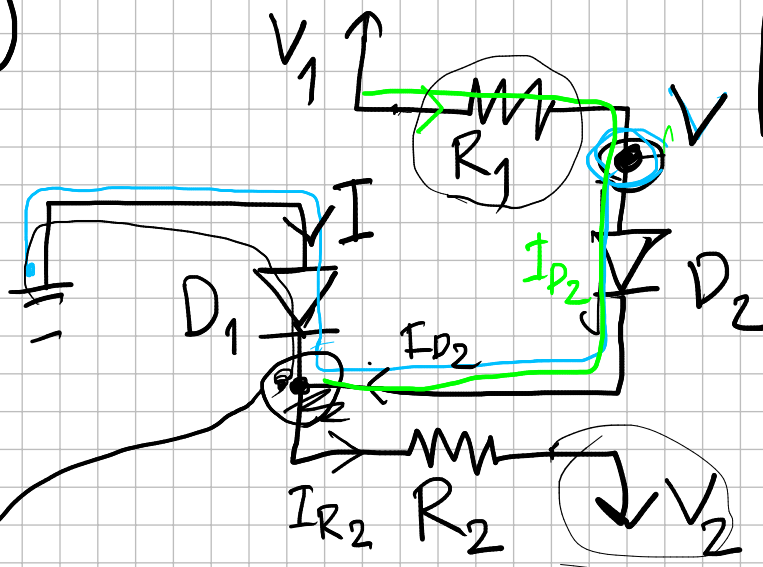

D_1, D_2 : ideal diode
 $R_1 = 5k\Omega$
 $R_2 = 10k\Omega$
 $V_1 = 20V$
 $V_2 = -50V$
 given

(ideal diode
 \Leftrightarrow voltage drop across the diode is 0V)

a) Find V : sol'n: $V = 0$ V


b) Find I : \rightarrow KCL: $I + I_{D2} = I_{R2}$

(Ohm's law R_1): $I_{D2} = \frac{V_1 - 0}{R_1} = \frac{V_1}{R_1}$

(Ohm's law R_2): $I_{R2} = \frac{0 - V_2}{R_2} = \frac{-V_2}{R_2}$

$$I = I_{R2} - I_{D2} = \frac{-V_2}{R_2} - \frac{V_1}{R_1} = \frac{50V}{10k\Omega} - \frac{20V}{5k\Omega}$$

$$= 5mA - 2mA = 3mA$$

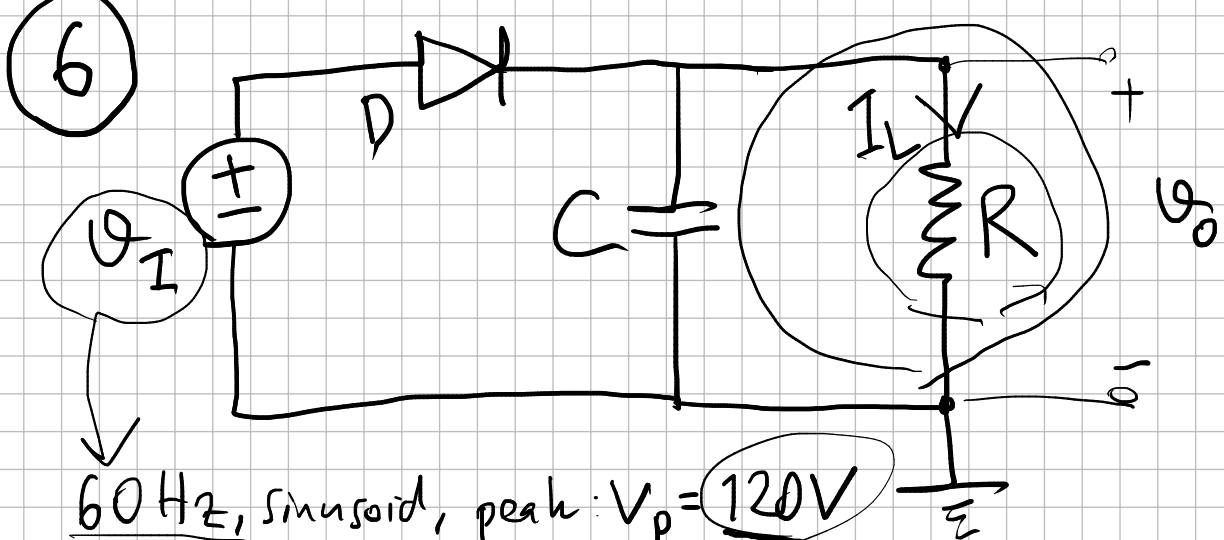

60 Hz, sinusoid, peak: $V_p = 120V$
 $R = 20 k\Omega$, D: diode ideal

a) Ripple voltage is 1V. Find C.

Solution:

$$V_r = \frac{V_p}{f \cdot C \cdot R} \rightarrow C = \frac{V_p}{V_r \cdot f \cdot R}$$

$$C = 7 \cdot 10^{-4} F$$

b) Find the fraction of the cycle during which diode is conducting.

Sol'n: conduction angle

$$\omega \cdot \Delta t = \sqrt{\frac{2 \cdot V_r}{V_p}}$$

$$\omega \cdot \Delta t = 0.1291 \text{ rad}$$

rad/s

$$\text{fraction} = \frac{0.1291 \text{ rad}}{2\pi \text{ rad}} = 2\%$$

c) Find the average value of diode current.

Solution:

$$i_{D_{av}} = I_L \left(1 + \pi \cdot \sqrt{2 V_p / V_r} \right)$$

(Ohm's law): $I_L = \frac{\hat{Q}_0}{R} = \frac{V_p}{R} = 6 \text{ mA}$

$\rightarrow i_{D_{av}} = 0.3 \text{ A}$